

Problem 3.2

a)

$$C = K\epsilon_0 \frac{A}{d}$$

b)

$$r = \rho \frac{d}{A}$$

c)

$$V(t) = \frac{Q(t)}{C}$$

$$I(t) = -\frac{dQ}{dt} = -\frac{V(t)}{r} = -\frac{Q(t)}{Cr}$$

Solve the separable differential equation:

$$\int \frac{1}{Q} dQ = \int \frac{1}{Cr} dt$$

$$\ln |Q| = -\frac{t}{Cr} + D$$

$$Q = De^{\frac{-t}{Cr}}$$

Given the initial value $Q(0) = Q_0$, $D = Q_0$.

$$\frac{1}{4}Q_0 = Q_0 e^{\frac{-t}{Cr}}$$

$$\ln \frac{1}{4} = \frac{-t}{Cr}$$

$$t = Cr \ln 4$$

Therefore $Cr \ln 4$ amount of time is required for the charge to decrease from Q_0 to $\frac{1}{4}Q_0$

d)

$$dE = I(t)^2 r dt = \left(\frac{dQ}{dt}\right)^2 r dt$$

$$= \left(-\frac{Q_0}{Cr} e^{\frac{-t}{Cr}}\right)^2 r dt$$

$$= \frac{Q_0^2}{C^2 r} e^{\frac{-2t}{Cr}} dt$$

e)

$$\begin{aligned} E &= \frac{Q_0^2}{C^2 r} \int_0^\infty e^{\frac{-2t}{Cr}} dt \\ &= \frac{Q_0^2}{C^2 r} \frac{C}{2r} (1 - e^{-\infty}) \\ &= \frac{1}{2} \frac{Q_0^2}{C} \end{aligned}$$

f)

The energy stored in a capacitor is $\frac{1}{2} \frac{Q_0^2}{C}$ when it is fully charged to Q_0 . It is the same as the total energy dissipated through the resistor calculated in **e**).